

# THE JIM WILLIAMS P A P E R S

## High-speed communications circuits

High-frequency communications signals need wideband analog circuits. High-speed monolithic amplifiers let you build simple, effective circuits to meet this need for both optical and RF transmission.

Jim Williams, *Linear Technology Corp*

**M**egahertz-range data transmission and communications requires wideband linear circuitry. By designing around a monolithic high-speed amplifier, you can easily implement a variety of standard high-performance communications circuits. The following circuits detail several such designs for both optical and RF transmission. All have been carefully worked out and can serve as good idea sources.

Amplifying fast photodiode signals over a wide range of optical intensity is one common optical-communications requirement. **Fig 1a's** fast FET amplifier gives wideband operation for 5 decades of photocurrent. You set up the photodiode in the conventional manner and use a  $-15V$  bias to aid diode response. Photocurrent feeds directly to  $IC_1$ 's summing point, which causes  $IC_1$ 's output signal to move to whatever level is required to maintain virtual ground at the negative input

pin. **Fig 1b** details the circuit's operating characteristics when using the HP5082-4204 photodiode.

You must use care when frequency-compensating this circuit. The diode has approximately 2 pF of parasitic capacitance, which creates a significant lag at  $IC_1$ 's summing point. Without a feedback capacitor, the circuit's high-speed dynamics are poor. **Fig 1c** illustrates this point by showing the circuit's response to a photocurrent input pulse (trace A) when the 3-pF feedback capacitor is removed.  $IC_1$ 's output voltage (trace B) overshoots and saturates before finally ringing down to its final value. Replacing the feedback capacitor gives **Fig 1d's** results. The same input pulse (trace A) produces a cleanly damped output voltage (trace B). The capacitor, however, imposes a 50% speed penalty (note that the horizontal scale of **Fig 1d** is faster than that of **Fig 1c**). This penalty is unavoidable because suppressing the parasitic ringing's relatively low frequency mandates significant roll-off.

### Basic amplifier has many uses

You can use the basic photodiode amplifier as the foundation for a variety of measurement and communications circuits. One such measurement circuit is **Fig 2a's** photointegrator. The output voltage represents the integral of the diode's photocurrent over a time period defined by the control line. This circuit is par-

# THE JIM WILLIAMS P A P E R S

ticularly useful for measuring the total energy in a light pulse or pulses. The circuit is a fast integrator and uses IC<sub>2A</sub> as a reset switch. IC<sub>2B</sub>, which the control input signal switches simultaneously with IC<sub>2A</sub>, compensates for IC<sub>2A</sub>'s charge-injection error.


When the control input line is low (**Fig 2b**, trace A) and no photocurrent is present, IC<sub>2A</sub> is closed and IC<sub>1</sub> acts as a grounded follower. Under these conditions, IC<sub>1</sub>'s output signal (trace C) sits at 0V. When the control input line goes high, IC<sub>1</sub> becomes an integrator as soon as IC<sub>2A</sub> opens. Due to the switch delay, IC<sub>2</sub> opens approximately 150 nsec after the control input line goes high.

When IC<sub>2A</sub> opens, it delivers some parasitic charge to IC<sub>1</sub>'s summing point. IC<sub>2B</sub> provides a compensatory charge-based pulse at IC<sub>1</sub>'s positive terminal to cancel

the effects of IC<sub>2A</sub>'s charge error. The combined effect of the two charge pulses shows up as a fast, small amplitude event in IC<sub>1</sub>'s output, which settles rapidly back to 0V. You can see this event on trace C near the 400-nsec mark.

Once the switches have opened, the integrator is ready to receive and record a light pulse. When a light pulse (trace B) falls on the photodiode, IC<sub>1</sub> responds by integrating (trace C). With the circuit as shown in **Fig 2a**, IC<sub>1</sub> integrates rapidly until the light pulse ceases. IC<sub>1</sub>'s voltage after the light event is over is related to the total energy the photodiode sees during the event. In typical operation, the control line then returns low, which resets IC<sub>1</sub> for the next light event.

When the circuit has only 10 pF of integration capacitance, its output droop rate is about 0.2V/ $\mu$ sec. You

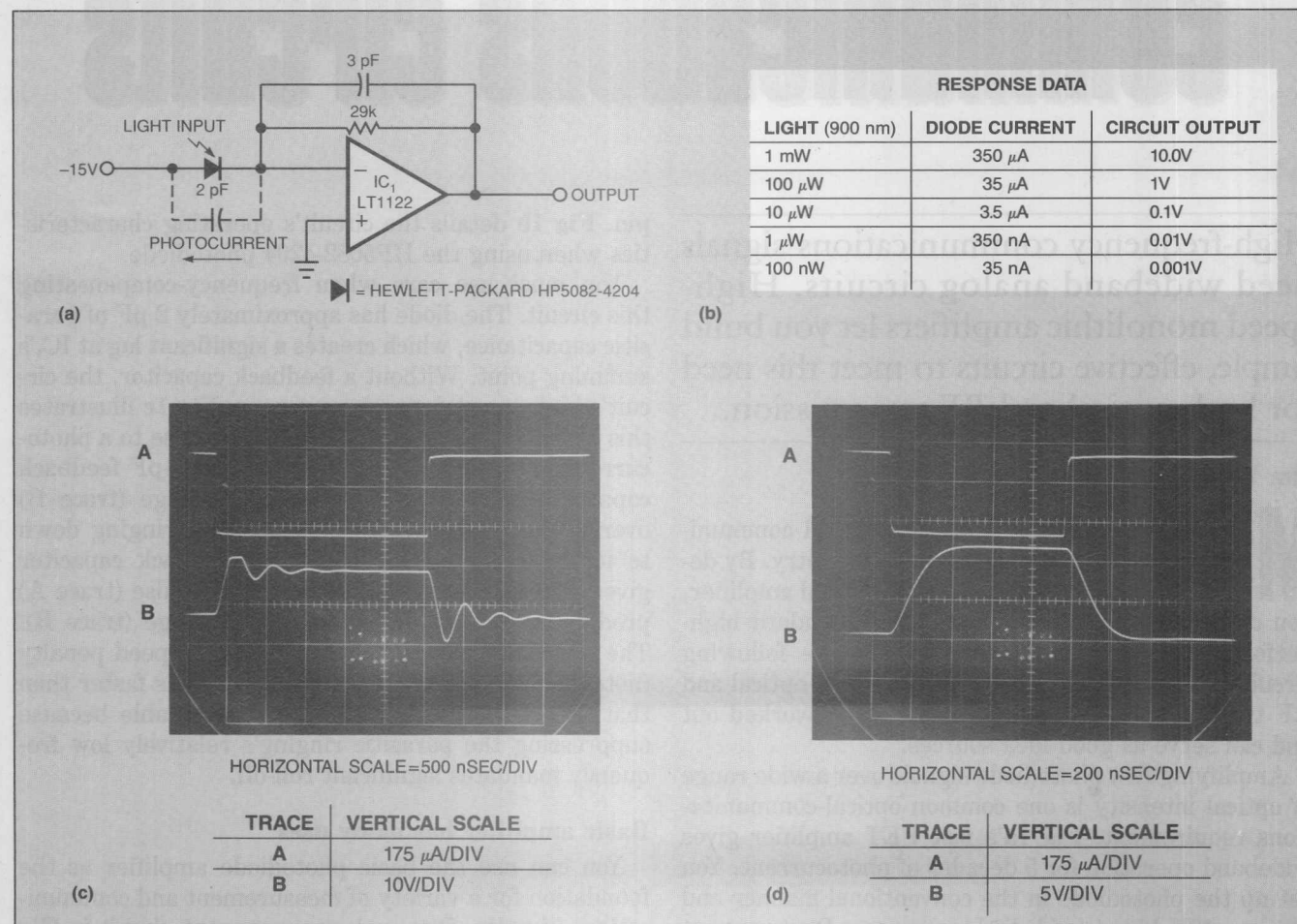


**Fig 1**—This basic photodiode amplifier circuit (a) handles 5 decades of light intensity. The table (b) details the circuit's operating characteristics with the HP5082-4204 diode. Parts c and d show the circuit's response (trace B) to an input signal (trace A) without and with compensation, respectively.

can increase the capacitance, but the integration speed will suffer accordingly. As shown, the circuit accommodates integration times of nanoseconds to milliseconds and photocurrents ranging from nanoamperes to hundreds of microamperes. Thus, light pulses with optical-power intensities spanning microwatts to milliwatts over wide ranges of duration are practical input signals.


The primary factors restricting the circuit's accuracy are  $IC_1$ 's 75-pA bias current and 12V output swing and

the effectiveness of the charge-cancellation network. Typically, the circuit can achieve full-scale accuracy within several percent if you trim the charge-cancellation network. To trim the network, make sure that no light falls on the diode while you repetitively pulse the control line. Adjust the trimmer capacitor to achieve a 0V output at  $IC_1$  immediately after the disturbance associated with the  $IC_{2A}$ - $IC_{2B}$  switching settles.

A communications circuit that relies on the basic photodiode amplifier is the simple fiber-optic receiver in Fig 3a.  $IC_1$ , a photocurrent-to-voltage converter similar to Fig 1a, feeds comparator  $IC_2$ .  $IC_2$  compares  $IC_1$ 's output voltage to a dc level established by the

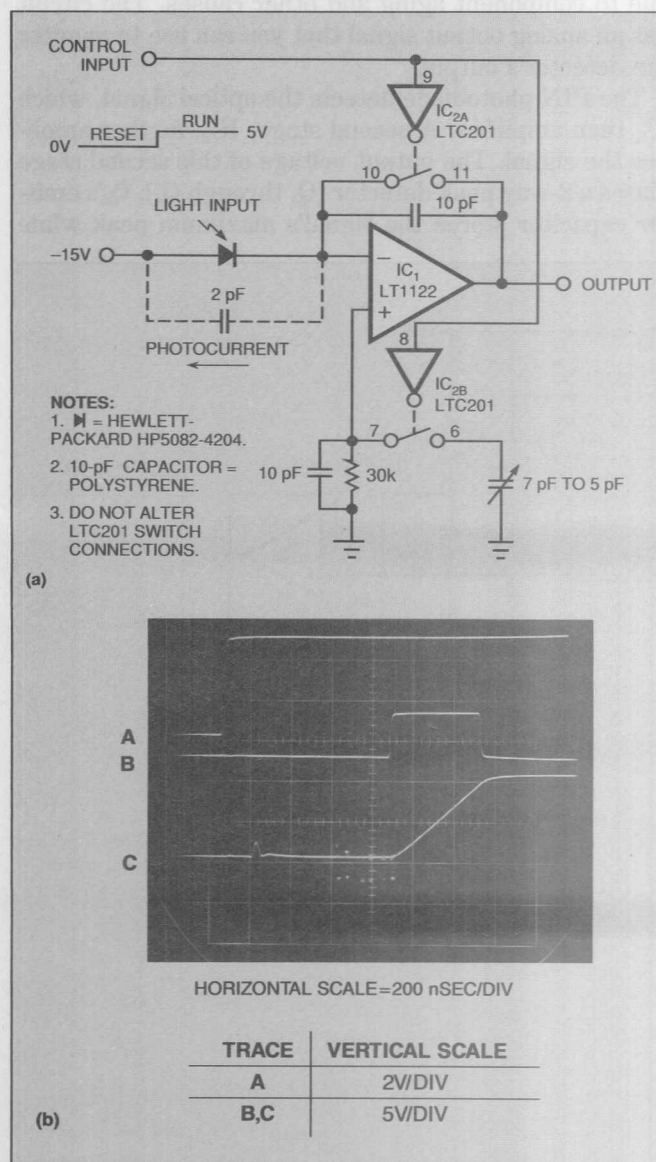

**Fig 2—The basic photodiode amplifier is the basis for this integrator, which has a resettable output (a). When the control line is high (b, trace A), the circuit integrates (trace C) the incoming signal (trace B).**

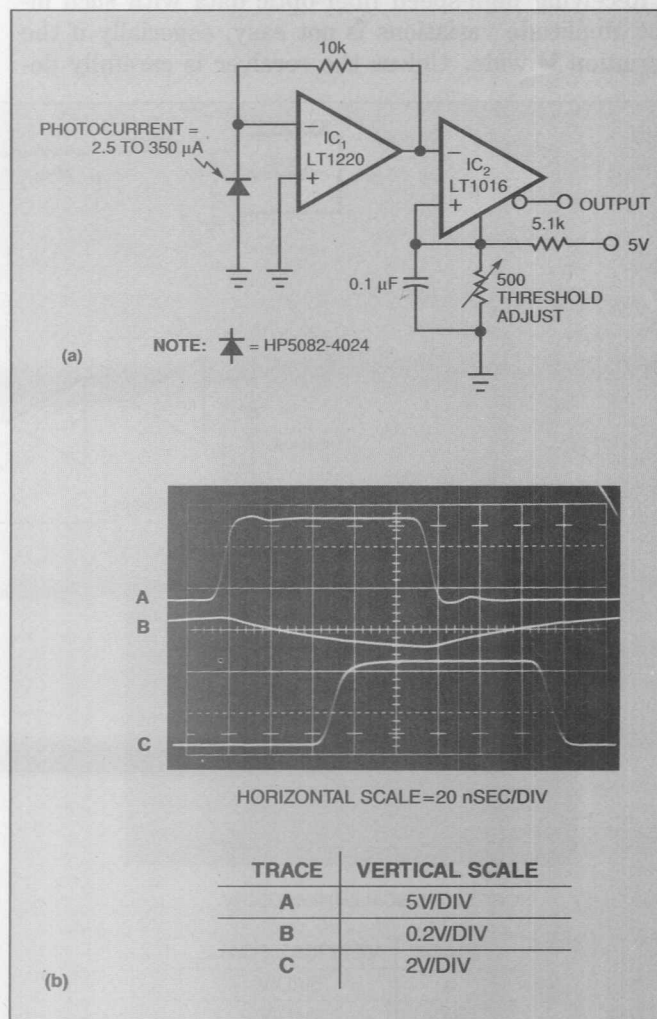

**Fig 3—This simple optical receiver (a) has a fixed signal threshold. The outputs of  $IC_1$  (b, trace B) and  $IC_2$  (trace C) lag the input signal (trace A).**




# THE JIM WILLIAMS P A P E R S

threshold-adjust potentiometer, thus producing a logic-compatible output signal. **Fig 3b** shows this circuit's typical waveforms. Trace A is a pulse associated with a light input signal. Trace B is IC<sub>1</sub>'s response, and trace C is IC<sub>2</sub>'s output signal. The phase shift between the photocurrent input signal and IC<sub>2</sub>'s output signal is due to IC<sub>1</sub>'s delay in reaching the threshold level. Reducing the threshold level will help reduce the shift but moves the circuit's operation closer to the noise floor. Additionally, the fixed threshold level cannot account for response changes in the emitter and detector diodes and the fiber-optic line over time and temperature. These response changes manifest as changes in the apparent amplitude of the signal.

Receiving high-speed fiber-optic data with such input amplitude variations is not easy, especially if the variation is wide. Unless the receiver is carefully de-

signed, the high-speed data and uncertain intensity of the light level can cause erroneous results. **Fig 4a** addresses the previous circuit's fixed-threshold limitation and offers significant performance advantages. This receiver reliably conditions fiber-optic input signals as fast as 40 MHz. The peak-to-peak amplitude of input signal can vary by as much as 40 dB. The circuit's digital output stage has an adaptive threshold trigger that accommodates signal intensity variations due to component aging and other causes. The circuit has an analog output signal that you can use to monitor the detector's output.

The PIN photodiode detects the optical signal, which IC<sub>1</sub> then amplifies. A second stage, IC<sub>2</sub>, further amplifies the signal. The output voltage of this second stage biases a 2-way peak detector (Q<sub>1</sub> through Q<sub>4</sub>). Q<sub>2</sub>'s emitter capacitor stores the signal's maximum peak while

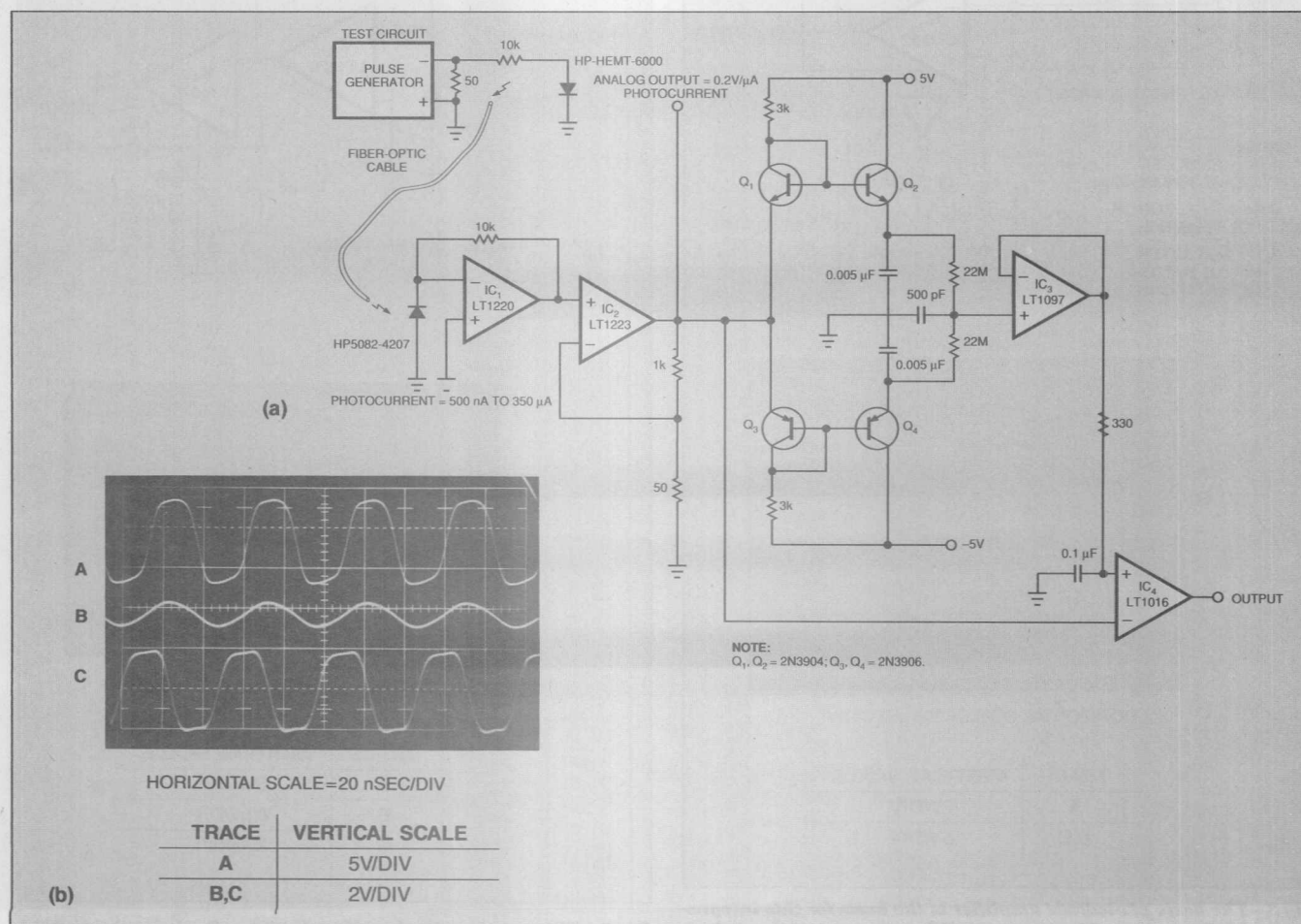

**Fig 4—A self-adapting threshold is the hallmark of this optical receiver (a). Driven by a test signal (b, trace A), the circuit lets you monitor the detector's current (trace B) in addition to producing a final output (trace C).**

## Protective circuit can save you a load


Some type of fuse or circuit breaker helps protect integrated circuits during developmental probing and expensive loads during trimming and calibration. **Fig Aa** shows a simple circuit that will turn off current in a load 18 nsec after that current exceeds a preset value. The circuit is especially versatile because one side of the load is grounded.

Under normal conditions,  $Q_1$ 's emitter is biased on and supplying power to the load via the 10 $\Omega$  current shunt. Differential amplifier  $IC_1$ 's output signal resides below comparator  $IC_2$ 's voltage-programmed trip point, and  $Q_2$  is off.

When an overload occurs,  $Q_1$ 's

emitter current begins to increase (**Fig Ab**, trace A, just prior to the third vertical division).  $IC_1$ 's output voltage (trace B) begins to rise as it tracks the increase in voltage across the 10 $\Omega$  shunt. The 9-k $\Omega$ , 1-k $\Omega$  voltage dividers keep  $IC_1$ 's input pins within their common-mode range.  $Q_1$ 's emitter voltage (trace C) begins to drop as the transistor beta-limits. When  $IC_1$ 's version of the load current exceeds  $IC_2$ 's trip point,  $IC_2$  goes high (trace D), which turns on  $Q_2$ . (Local positive feedback at  $IC_2$ 's latch pin causes  $IC_2$  to latch in this off state.)  $Q_2$  steals  $Q_1$ 's base drive, thus turning off the load current.

Once you've cleared the load fault, you can use the push button to reset the circuit. The delay from the onset of excessive load current to complete circuit shut-down is less than 18 nsec. (When interpreting the **Fig Ab** waveforms, note that trace A's current probe has a 4-nsec delay.) To calibrate the circuit, ground  $Q_2$ 's base and install a 250-mA load. Adjust the 200 $\Omega$  trim for a 2.5V output signal at  $IC_1$ . Next, remove the load, unground  $Q_2$ 's base, and press the reset button. Finally, set the desired trip voltage, and the circuit is ready for use.

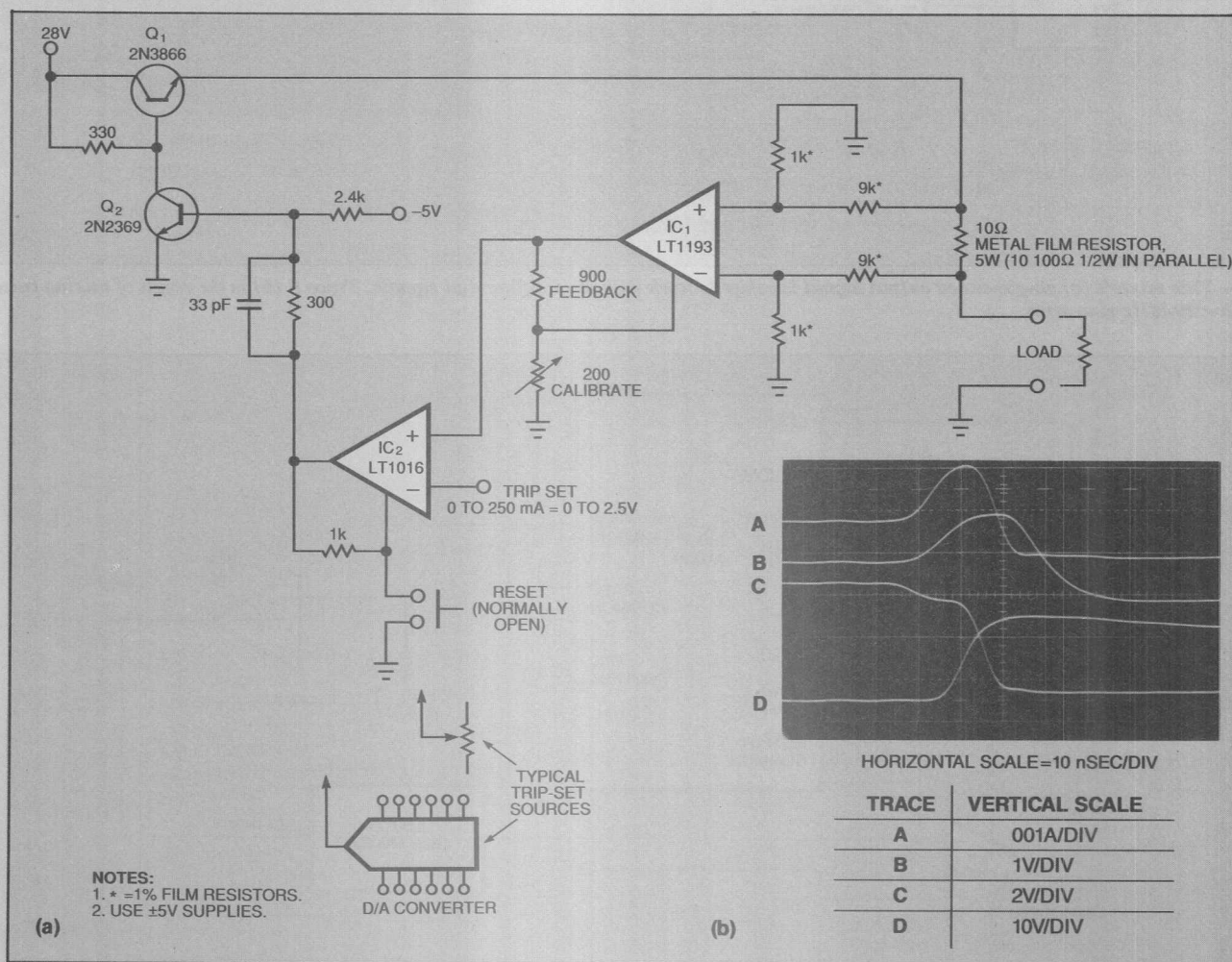


**Fig A—This circuit breaker (a) trips in as little as 18 nsec. The circuit shuts down the load (b, trace C) when the load current (trace A) exceeds the trip point. Trace B represents  $IC_1$ 's output voltage; trace D represents  $IC_2$ 's output voltage.**

# THE JIM WILLIAMS P A P E R S


$Q_4$ 's emitter capacitor retains the minimum excursion. The dc value of the midpoint of  $IC_2$ 's output signal appears at the junction of the 500-pF capacitor and the 22-M $\Omega$  resistors. This point will always be midway between the signal's excursions, regardless of the signal's absolute amplitude. The low-bias LT1097 op amp ( $IC_3$ ) buffers this signal-adaptive voltage to set the

trigger voltage at  $IC_4$ 's positive input pin.  $IC_4$ 's negative input pin is biased directly from  $IC_2$ 's output.

Fig 4b shows the results of using the test circuit of Fig 4a. The pulse generator's output signal is trace A;  $IC_2$ 's analog output voltage is trace B.  $IC_4$ 's output signal is trace C. The waveforms were recorded using a 5- $\mu$ A photocurrent at about 20 MHz as the test signal.

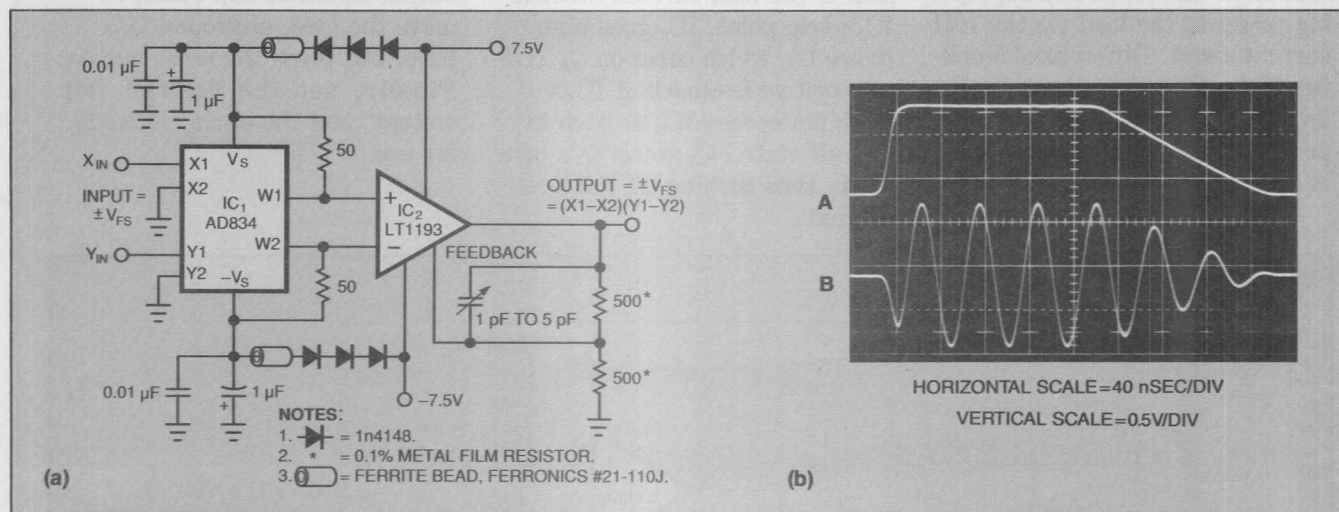

**Fig 5—This mixer's (a) single-ended output signal is easier to work with than differential signals. Trace B (b) is the result of mixing trace A with a 20-MHz sine wave.**

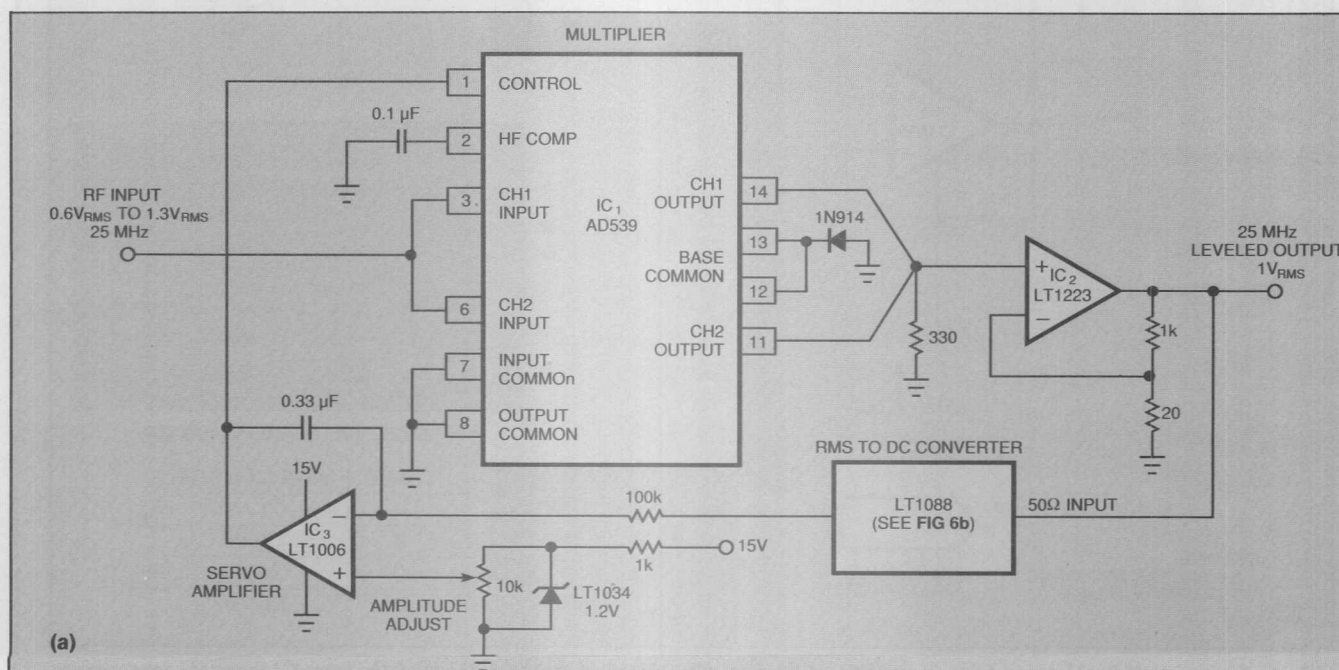

**Fig 6—A servo loop enables this circuit to stabilize RF signals. The loop circuit (a) uses an rms-to-dc converter (b).**



Note that IC<sub>4</sub>'s output transitions (trace C) correspond with the midpoint (plus IC<sub>4</sub>'s 10-nsec propagation delay) of IC<sub>2</sub>'s output signal (trace B), in accordance with the adaptive-trigger circuit's operation.

### Mixer yields single-ended signal

Another common communications requirement, particularly for RF work, is mixing signals for modulation or heterodyning. Analog multipliers can mix signals, but they have a drawback; their output signals take a differential form. These differential signals, which have substantial common-mode content, are frequently inconvenient to work with. You can use RF transformers to convert them to single-ended signals, but you lose dc and low-frequency information in the process. Fig 5a illustrates a better approach. The circuit uses the LT1193 differential amplifier (IC<sub>2</sub>) to accomplish the differential-to-single-ended transition. Set up IC<sub>1</sub> in the configuration Ref 1 recommends. The LT1193 takes the differential signal from IC<sub>1</sub>'s 50 $\Omega$ -terminated output lines and provides a single-ended output signal. The amplifier's gain of 2 yields an 11V output signal at full scale.

IC<sub>1</sub>'s output signals ride on a common-mode level quite close to the device's positive supply. This common-mode level falls outside IC<sub>2</sub>'s input common-mode


### Acronyms used in this article

FET—Field-effect transistor  
RF—Radio frequency  
rms—Root mean square

range. The diodes in the 7.5V supply rails drop the supply voltage to IC<sub>1</sub>, which biases IC<sub>1</sub>'s output signals within IC<sub>2</sub>'s input range. This scheme avoids the attenuation and matching problems you'd get if you placed a level shift between the multiplier and amplifier. The impedance of the ferrite beads combine with the diodes' impedance to ensure adequate bypassing for the multiplier.

This circuit's performance is quite impressive. Error remains within 2% over dc to 50 MHz, and feedthrough is less than -50 dB. Trimming the circuit involves adjusting the variable capacitor at the amplifier for minimal output square-wave peaking. Fig 5b shows the circuit's performance when multiplying a 20-MHz sine wave by trace A's waveform. The output signal (trace B) is a singularly clean instantaneous representation of the X and Y input products.

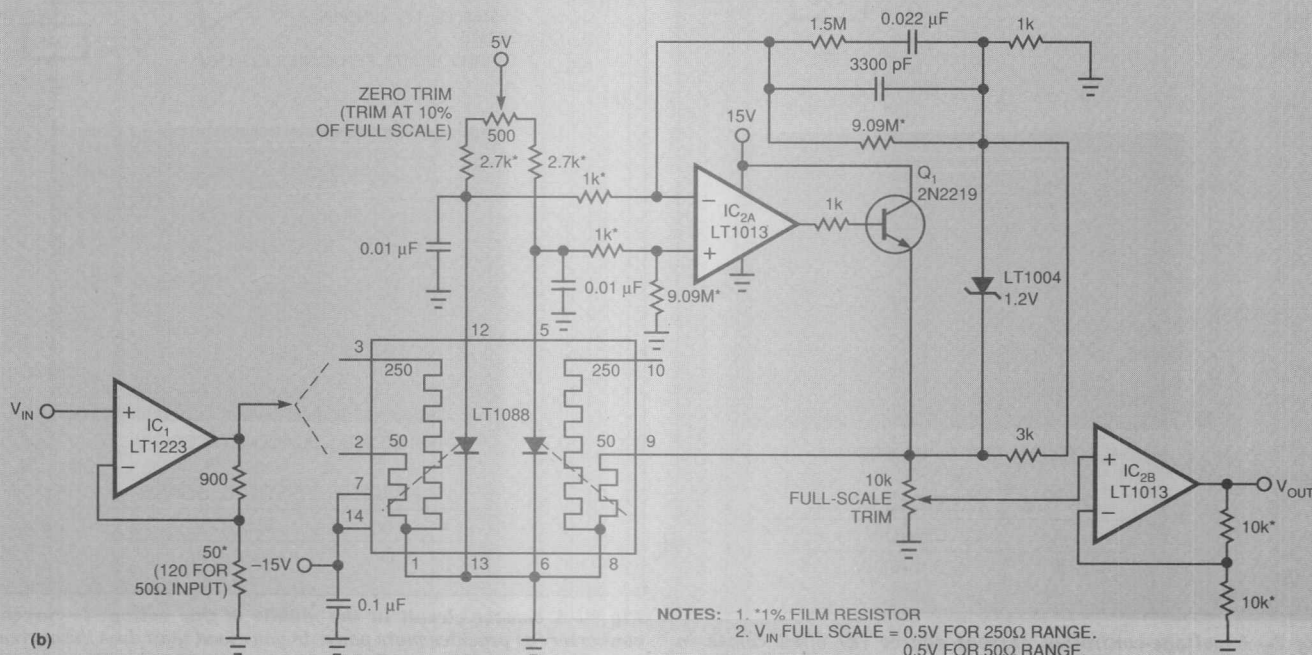Often in RF communications you will want to stabilize the amplitude of a waveform against variations in




# THE JIM WILLIAMS P A P E R S

input signal strength over time and temperature. Instruments and transmitters must often provide this function, which is not easy if the instruments must also maintain waveform purity. **Fig 6a** shows a circuit that stabilizes waveform amplitudes while maintaining waveform purity.


You apply the RF input signal to the AD539 wideband multiplier ( $IC_1$ ), which drives  $IC_2$ . An LT1088-based rms-to-dc converter (**Fig 6b**) turns  $IC_2$ 's output to dc. A servo amplifier ( $IC_3$ ) compares that dc output signal with a settable dc reference and biases the multiplier's control channel, thus completing a loop. The 0.33- $\mu$ F capacitor provides frequency compensation by rolling off gain at a frequency well below the response of the LT1088 servo amplifier. The loop maintains the output's 25-MHz rms amplitude at the dc reference's

value; it rejects changes in load, input-signal strength, power-supply voltage, and other variables.

All of the previous circuits have a voltage-based output signal. Sometimes, however, you'll want your output in current form. **Fig 7a** shows a voltage-controlled current source that has both the load and control voltage referenced to ground. This simple, powerful circuit produces output current in accordance with the sign

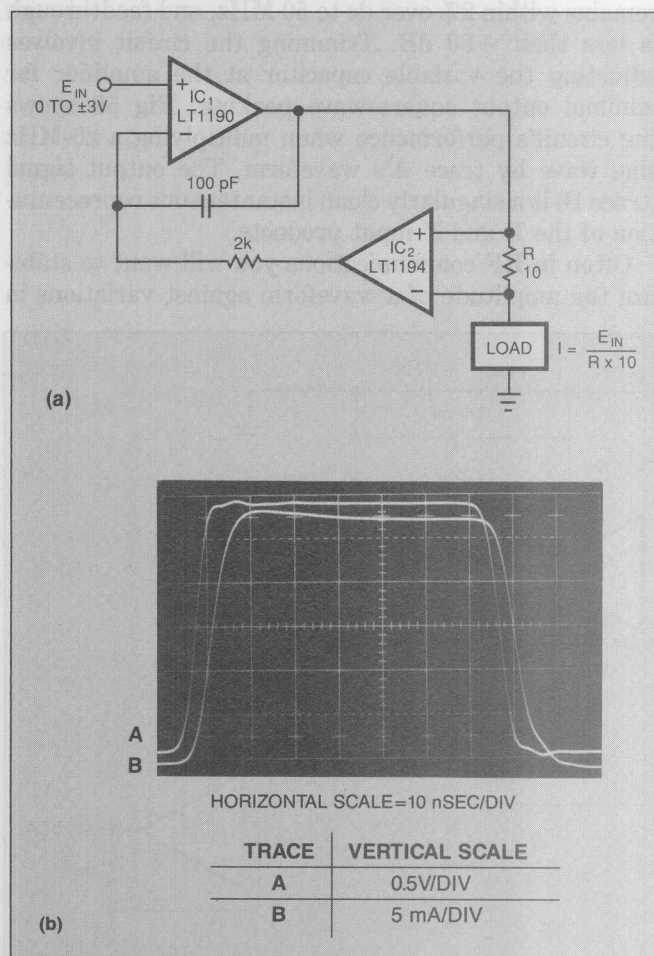

**Fig 7**—A voltage-controlled current source (a) often comes in handy. This circuit produces a clean output current (b, trace B) 4 nsec after the input voltage (trace A).

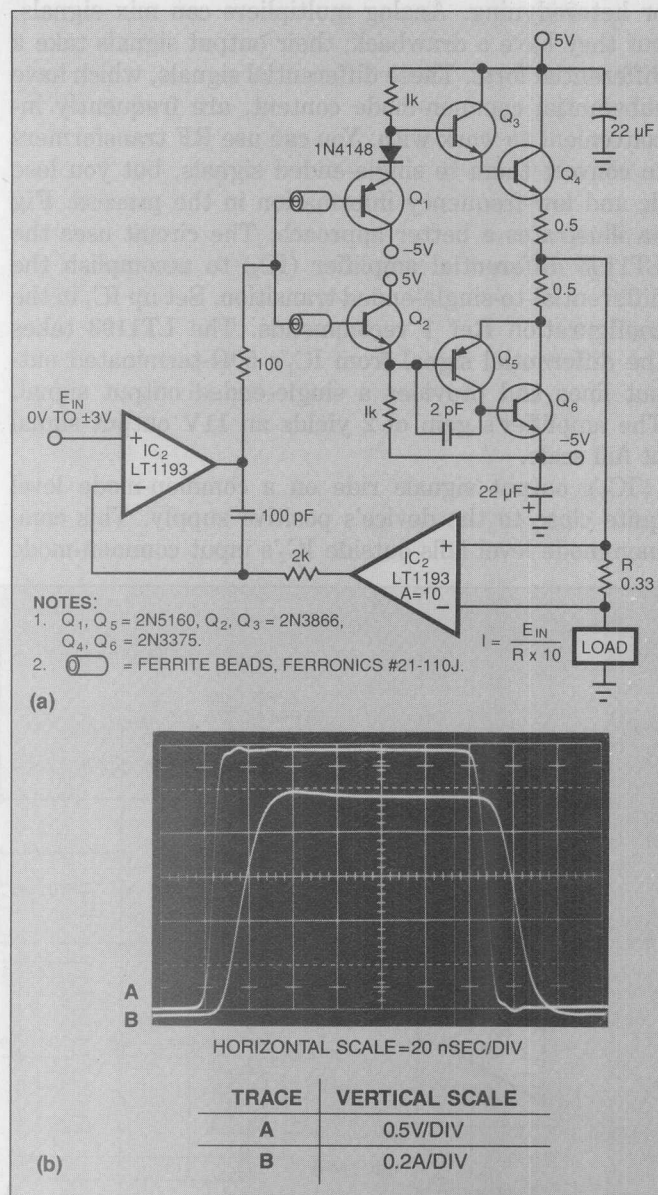

**Fig 8**—A booster circuit in the middle of this voltage-to-current converter (a) provides more power to your load than does the current source of **Fig 7**. Trace A (b) represents voltage; trace B represents current.



and magnitude of the control voltage. Resistor R sets the circuit's scale factor.

IC<sub>1</sub>, biased by E<sub>IN</sub>, drives current through R (in this case 10Ω) and the load. IC<sub>2</sub>, sensing the differential voltage across R, closes a loop back to IC<sub>1</sub>. The load current is constant because IC<sub>1</sub>'s loop forces a fixed voltage across R. The 2-kΩ, 100-pF combination sets roll-off, and the configuration is stable. Fig 7b shows the circuit's dynamic response. Trace A is the control input voltage, E<sub>IN</sub>; trace B is the output current. The response has a delay of 5 nsec and no slew residue or aberrations.

Fig 8a is Fig 7a's basic current source plus a 1A booster stage to increase output power. Including the booster inside IC<sub>1</sub>'s feedback loop eliminates the booster's dc errors. Note that the booster needs no current-limiting features because of the circuit's inherent current-limiting operation. Fig 8b shows that the circuit's response is as clean as that of the lower-power version, although its delay is about 20 nsec slower. The loop stability considerations involved in placing IC<sub>2</sub> and the booster in IC<sub>1</sub>'s feedback path are significant. This type of circuit receives detailed treatment in Ref 2.

**EDN**

## References

1. Analog Devices Inc, *Linear Products Databook*, AD834 Datasheet, pgs 6-43.
2. Williams, Jim, "Subduing high-speed op-amp problems," *EDN*, October 24, 1991, pg 135.

## Author's biography

For more information on this article's author, turn to pg 163 in the October 10, 1991 issue.

Article Interest Quotient (Circle One)  
High 497 Medium 498 Low 499

## LAMB® DC Motors add speed control and reliability to pumps

These 12-24 VDC brushless motors give you controllability for smart pumping applications. Either 2.0" or 3.2" diameters, with stall torque to 84 oz-in, puts high power in a compact package. And, no brushes to wear means more reliable operation. AMETEK, Lamb Electric Division, 627 Lake Street, Kent, OH 44240. Tel: 216-673-3451. Fax: 216-673-8994. In Europe, Friedrichstrasse 24, 6200 Wiesbaden, Germany. Tel: 611-370031. Fax: 611-370033.

**AMETEK**  
LAMB ELECTRIC DIVISION


CIRCLE NO. 158

## THE SILENT CHALLENGER

TASCO Electronics, a recognized leader of digital technology in Japan, is introducing a new and exceptionally silent integrated thermal driver, for installation in many OEM products. The amazingly quiet (70dB) and unparalleled high speed (maximum 300 LPM), reproduces the finest graphic details. Its compact and maintenance free carriage is a gift any design engineer will be thrilled receiving and put to good use in a hurry.

The PE-525 being introduced to the world market is worthy of your most critical acclaim. Call now for more information about the SILENT CHALLENGER.

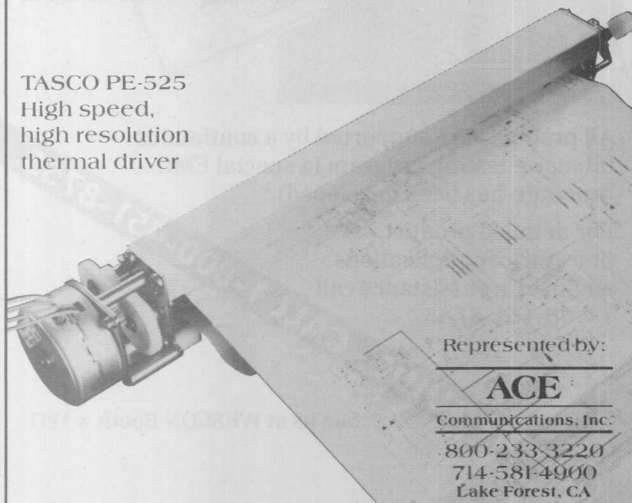TASCO PE-525  
High speed,  
high resolution  
thermal driver



Represented by:

**ACE**

Communications, Inc.

800-233-3220  
714-581-4900  
Lake Forest, CA

TASCO Electronics Co., Ltd.  
38 Minamiyouchi, Higashibata, Anjyo, JAPAN  
Tel 81-566-92-4103 Fax 81-566-92-3108

CIRCLE NO. 159